

# Verilog Tutorial

## Combinational Logic


Shutha Pulendran

October 3, 2016
 
# Understanding Verilog

- Verilog is a **hardware description language** (HDL), **NOT a programming language!!**
- It's used to describe how a circuit must look like


**Useful for describing  
complex circuits**



# Modules in Verilog

- Each module represents a logic circuit
  - Think of it as a black box with inputs and outputs
  - The relationships between these inputs and outputs are defined inside the module
- Separate modules can be connected to make large, complex circuits

# A sample module

 


```
module mycircuit (a,b,c,y1,y2); // specify inputs and outputs
    input  a,b,c;    // identify the inputs
    output y1,y2;    // identify the outputs


    // implement the logic functionality below
    assign y1  = a & b;
    assign y2  = (a & b) | (~b & c);
endmodule
```
 
# Wires in Verilog

- They represent physical wires (connections) in a circuit, i.e., connecting two points in a circuit (similar to wires used in Lab 1)
- Commonly used to name internal connections other than inputs and outputs



# The same code using wires

 

```
module mycircuit (a,b,c,y1,y2); // specify inputs and outputs
    input  a, b, c;           // identify the inputs
    output y1, y2;           // identify the outputs
    wire  w1, w2, w3;        // identify internal connections

    assign w1 = ~b;
    assign w2 = w1 & c
    assign w3 = a & b;


    assign y1 = w3;
    assign y2 = w2 | w3;
endmodule
```

# Points to Remember

- **Ordering of Verilog statements doesn't matter** because they represent circuit connections
- As long as the statements describe a complete circuit, the code is good
- Verilog statements don't get executed in a computer similar to other programming languages (e.g., C/C++)
- Always think in terms of building actual hardware connections with wires (e.g., Lab 1 )
 
# Top-Level Module


- Top-Level module is the largest black box that contains all of your circuits
- Must be named the same as your project in Quartus
- Only **one top-level module** can exist in a project and must be defined
- Can have many submodules




 
# Module Instantiation

- Useful when the same module (same logic circuit) can be used multiple times as submodule
- Example



- 3-bit input and 2-bit output

# Code For Module Instantiation


- Our previous circuit ("mycircuit") is repeated two times

```
module mytop(in, out); // top-level module
    input [2:0] in;
    output [1:0] out;
    wire connector1, connector2;

    mycircuit myc1 ( //submodule 1
        .a(in[0]),
        .b(in[1]),
        .c(in[2]),
        .y1(connector1),
        .y2(connector2),
    );

    mycircuit myc2 ( //submodule 2
        .a(connector1),
        .b(connector2),
        .c(in[2]);
        .y1(out[0]),
        .y2(out[1]),
    );

endmodule
```

 

```
module mycircuit (a,b,c,y1,y2);
    input  a,b,c;
    output y1,y2;

    assign y1 = a & b;
    assign y2 = (a & b) | (~b & c);
endmodule
```

# Constants in Verilog

- Format: <bitwidth>'<base><number>

No. of bits for the constant

Base number system  
h – hexadecimal  
b – binary  
d – decimal

The constant

Example:

// All these assignments are equal

```
assign a = 5'd17;
```

```
assign a = 5'b10001;
```

```
assign a = 5'h11;
```

# Bus Structure Definition & Implication

- The method of defining bus structure is important

```
wire [2:0] a; // 3-bit
wire [3:1] b; // 3-bit
wire c; // 1-bit
```



```
assign a=b; ⇔ a[0] = b[1]; a[1]= b[2]; a[2] = b[3];
assign b=a; ⇔ b[1] = a[0]; b[2] = a[1]; b[3] = a[2];
assign c=a; ⇔ c = a[0];
assign a = 3'd7; ⇔ a = 3'b111; ⇔ a = 3'h7;
```

# Behavioural Verilog using always block

- No **assign** statements inside **always** block
- All **if** must have corresponding **else**, i.e., all behaviours must be defined

```
module behavior_example (a, b, out);  
input a,b;  
output reg out; //reg is an output wire inside always block  
    always @(*) // for changes in any of the signals  
        begin  
            if ( a==0 && b==0)  
                out = 1'b0;  
            else if (a==0 && b==1)  
                out = 1'b0;  
            else if (a==1 && b==0)  
                out = 1'b0;  
            else  
                out = 1'b1;  
        end  
endmodule
```

# Results

 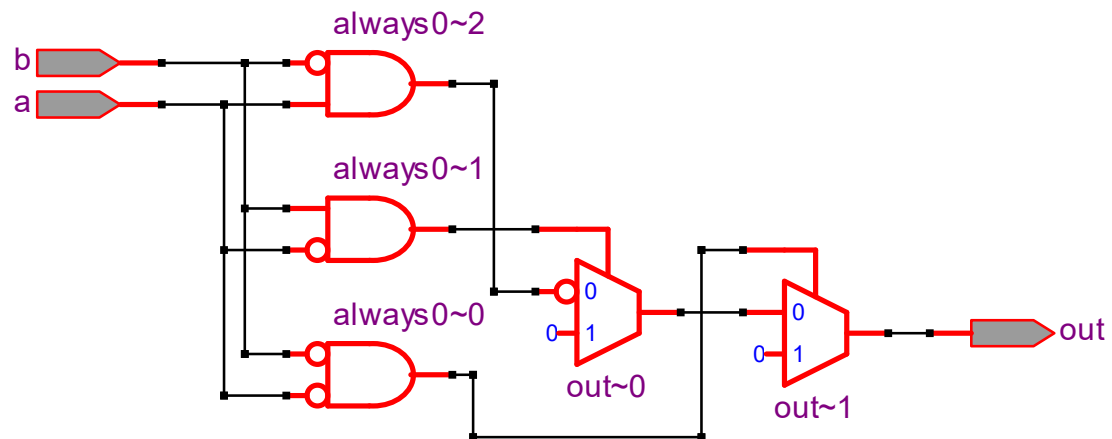

# Simplified Description

- Describes the same logic given previously

```
module behavior_example_simplified (input a, input b, output
reg out);
    always @(*)
        begin
            if ( a==1 && b==1) // can write if ({a,b} ==2b'11)
                out = 1'b1;
            else
                out = 1'b0;
        end
    endmodule
```



# Case Statement

- The same functionality using a case statement

```
module case_example (input a, input b, output reg out);  
    always @(*)  
        begin  
            case ({a,b})  
                2'b00: out=1'b0;  
                2'b01: out=1'b0;  
                2'b10: out=1'b0;  
                2'b11: out=1'b1;  
            endcase  
        end  
endmodule
```



# Case Statement Variation

- An Another variation for the same circuit

```
module case_example_variation (input a, input b, output reg
out);
    always @(*)
        begin
            case ({a,b})
                2'b11: out=1'b1;
                default: out=1'b0;
            endcase
        end
endmodule
```

# Important Points

- The fastest circuit is produced by  
`assign out = a & b;`
- Cannot instantiate a module within an  
`always` block
- Don't write multiple `assign`  
statements or `always` blocks driving  
the same wire or reg
- Verilog is **CASE SENSITIVE!**

# Summary

- Understanding Verilog for combinational logic
- Verilog Modules
- Defining and using `wire`
- Top-level module and submodules
- Module instantiation for multiple submodules
- Defining constants and bus structures
- Behavioural Verilog using `always` block
  - Using `if ... else` statements
  - Using `case` statements
  - Using `reg` for `always` block output