

# Verilog Tutorial

## Sequential Logic & FSM


Shutha Pulendran

October 24, 2016

# Verilog Recap

- Verilog is a **hardware description language**
- **Module** - describes logic circuit
- **Wire** - an internal connection within a module
- **Top-level module** - the largest module that contains all of the circuits
- **Module instantiation** - used for multiple submodules
- Verilog is **case sensitive**
- Defining **constants** and **bus structures**
- Behavioural Verilog using **always** block
  - Using **if ... else** statements
  - Using **case** statements
  - Using **reg** for always block output


# Positive-Edge Triggered D Flip-Flop

 

```
module d_flipflop_pos(input clk, input d, output reg Q);  
    always @(posedge clk) //Notice the keyword posedge  
        begin  
            Q <= d; // Notice the operator <=  
        end  
endmodule
```


- Use **<=** for edge-triggered **always** block
- Use **=** for **always(\*)** block

# Negative-Edge Triggered D Flip-Flop

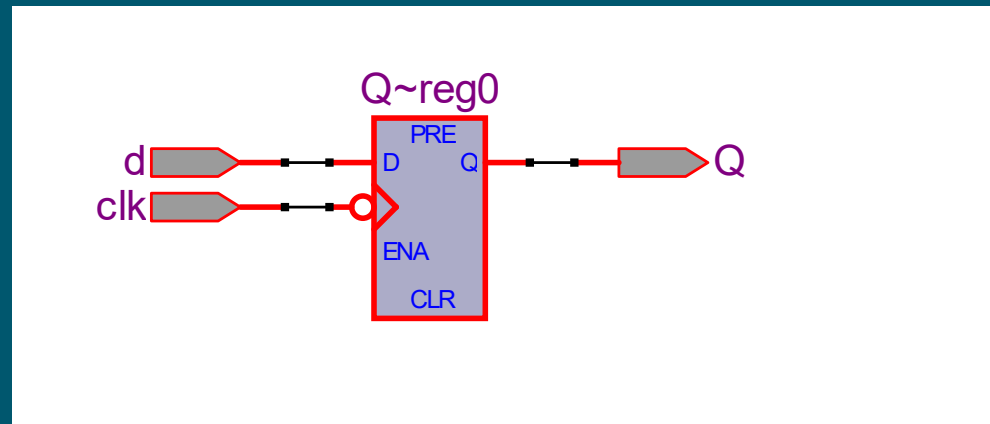


```
module d_flipflop_neg(input clk, input d, output reg Q);  
    always @(negedge clk) //notice the keyword negedge  
        begin  
            Q <= d;  
        end  
endmodule
```

# Review - Reset Notation

 

Synchronous  
clear  
(active high)

Asynchronous  
clear  
(active high)

 


Synchronous  
clear  
(active low)

Asynchronous  
clear  
(active low)


from course notes

# D Flip-Flop with Asynchronous Reset

 


```
module d_flipflop_reset(input clk, input d, input reset,
output reg Q);
    always @(posedge clk or posedge reset)
        begin
            if (reset == 1'b1)
                Q <= 1'b0;
            else
                Q <= d;
        end
endmodule
```
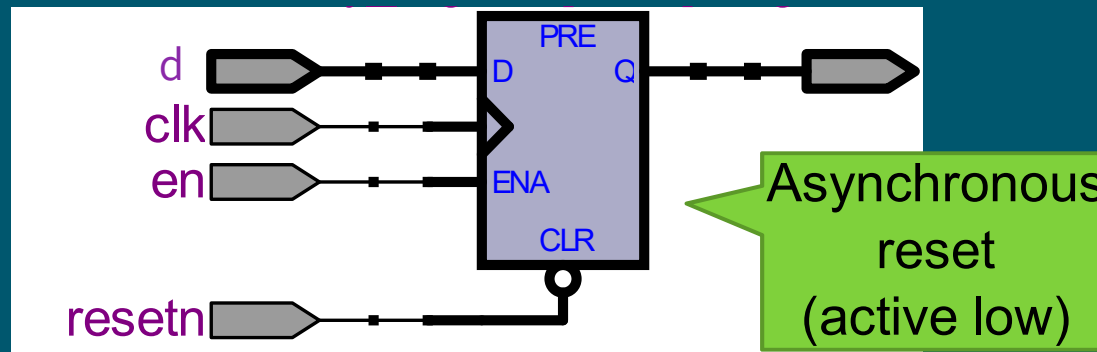
# D Flip-Flop with Enable and Asynchronous reset



```
module d_flipflop_enable(input clk, input d, input reset, input
en, output reg Q);
    always @(posedge clk, negedge reset)
        begin
            if (reset == 1'b0)
                Q <= 1'b0;
            else if (en = 1'b1)
                Q <= d;
            else
                Q <= Q; // These two lines are not needed
        end
endmodule
```

# Verilog Code ?

 

Note Asynchronous reset  
(active low)



# Solution 1 - Using Module Instantiation

```
module main_circuit1 (input clk, input reset_n, input [1:0] in, output out);

    wire q1, q2, and_out;

    d_ff ff1(.clk(clk), .d(in[0]), .reset_n(reset_n), .Q(q1));
    d_ff ff2(.clk(clk), .d(in[1]), .reset_n(reset_n), .Q(q2));
    d_ff ff3(.clk(clk), .d(and_out), .reset_n(reset_n), .Q(out));

    assign and_out = q1 & q2;

endmodule
```

```
module d_ff(input clk, input d, input reset_n, output reg Q);

    always @(posedge clk, negedge reset_n)
        begin
            if (reset_n == 1'b0)
                Q <= 1'b0;
            else
                Q <= d;
            end
        end

endmodule
```

# Solution 2 - Using two always block

```
module main_circuit2 (input clk, input [1:0] in, input reset_n, output reg out);

reg [1:0] Q; // For the output of the first two flipflops
wire and_out; // for the and gate output

always @ (posedge clk, negedge reset_n) // the first two flipflops
begin
    if(reset_n==1'b0)
        Q <= 2'b00;
    else
        Q <= in;
    end

always @ (posedge clk, negedge reset_n) // the last flipflop
begin
    if(reset_n==1'b0)
        out <= 1'b0;
    else
        out <= and_out;
    end

assign and_out = Q[0] & Q[1];

endmodule
```

# Solution 3 – Using one always block

```
module main_circuit3 (input clk, input [1:0] in, input reset_n, output reg out);

reg [1:0] Q; // For the output of the first two flipflops
wire and_out; // for the and gate output

    always @ (posedge clk or negedge reset_n) // Implement all flipflops in one
always block. Note all flipflops have the same clock and reset_n signals
    begin
        if(reset_n==1'b0)
            begin
                Q <= 2'b00;
                out <= 1'b0;
            end
        else
            begin
                Q <= in;
                out <= and_out;
            end
        end

    assign and_out = Q[0] & Q[1];

endmodule
```

# Solution 3 – Another Variation

```
module main_circuit4 (input clk, input [1:0] in, input reset_n, output out);

reg [2:0] Q; // For the output of all flipflops
wire and_out; // for the and gate output

always @ (posedge clk, negedge reset_n) // Implement all flipflops in one
always block
begin
    if(reset_n==1'b0)
        Q <= 3'b000;
    else
        Q <= {and_out, in};
    end

assign out = Q[2];
assign and_out = Q[0] & Q[1];

endmodule
```

# Combinational Vs. Sequential

## Combinational Logic

- Use `always@(*)` block
- Use blocking assignments using `=` operator
- All cases must be specified inside the `always` block, e.g., `case` statement must contain a `default` statement

## Sequential Logic


- Use edge-triggered `always` block, i.e., `always@(posedge ..)`, `always@(negedge ...)`
- Use non-blocking assignments using `<=` operator

**ORDERING OF `always` blocks DOES NOT MATTER!!!**

# Important Verilog Tips

- Don't use `posedge` and `negedge` for the same signal inside an `always` block, e.g.,  
`always @(posedge clk, negedge clk)`
- Don't define multiple `always` blocks assigning values to the same `reg`
- Don't mix blocking (`=`) and nonblocking (`<=`) assignments within the same `always` block
- You can use spacers for constants for clarity, e.g.,  
`8'b1001_0001`

# Review - Finite State Machines

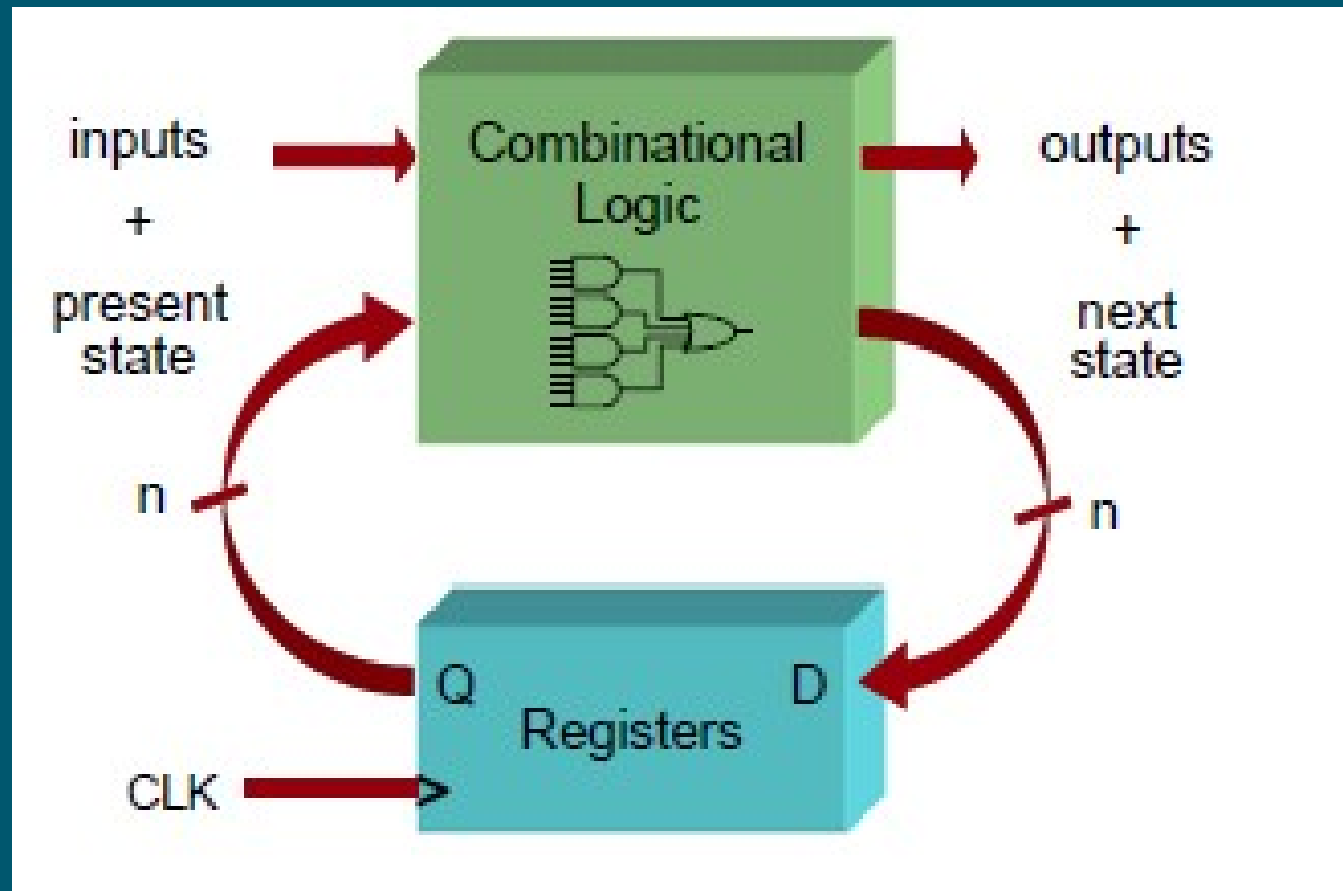

Source: MIT Course Notes, 2012

# FSM Design Procedure

1. Draw state diagram and state transition table
2. State Assignment
3. Minimize logic and circuit design (not required for some type of Verilog implementation)
4. Implement the design in Verilog



# Example: Vending machine FSM

- Let's build a simple vending machine
  - User can put in a nickel (5¢) or a dime (10¢)
  - The cost of the pop is 10¢
  - Dispense the pop when the amount entered is sufficient (10¢ or more), and produce appropriate change if necessary.



# Inputs and Outputs

- Inputs: {Nickel (N), Dime (D)}
  - $N=1$  for Nickel, input  $\rightarrow 10$
  - $D=1$  for Dime, input  $\rightarrow 01$
  - Both N and D will never be 1 at the same time (Don't care)
- Outputs: {Dispensing the pop (P), change (C)}
  - $P=1$  will trigger mechanism for dispensing pop
  - $C=1$  will trigger mechanism for dispensing change
  - Dispense pop only, output  $\rightarrow 10$
  - Dispense change only, output  $\rightarrow 01$
  - Dispense both, output  $\rightarrow 11$


# State Diagram

## Moore Type

Inputs: {N, D}

Nickel = 5¢, Dime = 10¢

Outputs: {P, C}

 

# State Table – Moore Type

Present State ( $Q_1 Q_0$ )	Input {N,D}	Next State ( $D_1 D_0$ )	Output {P,C}
S0 (00)	00	S0 (00)	00
	01	S10 (10)	
	10	S5 (01)	
S5 (01)	00	S5 (01)	00
	01	S15 (11)	
	10	S10 (10)	
S10 (10)	00	S0 (00)	10
	01	S10 (10)	
	10	S5 (01)	
S15 (11)	00	S0 (00)	11
	01	S10 (10)	
	10	S5 (01)	

$Q_1 Q_0 \backslash ND$	00	01	11	10
00	0	1	X	0
01	0	1	X	1
11	0	1	X	0
10	0	1	X	0

$Q_1 Q_0 \backslash ND$	00	01	11	10
00	0	0	X	1
01	1	1	X	0
11	0	0	X	1
10	0	0	X	1

# Logic Expressions

$$D_1 = D + NQ_0\overline{Q_1}$$

Next States

$$D_0 = NQ_1 + N\overline{Q_0} + \overline{N}\overline{Q_1}Q_0$$

$$P = Q_1$$

$$C = Q_1Q_0$$

Outputs

# Verilog - Solution 1

```
module vending_machine(input N, input D, input reset_n, input clk,
output P, output C);
wire [1:0] next_state;
reg [1:0] present_state;

always @ (posedge clk, negedge reset_n) // Implement flipflops in one
always block.
begin
    if(reset_n==1'b0)
        present_state <= 2'b00;
    else
        present_state <= next_state;
end

// Implement combinational logic (logic expressions)
assign next_state[1] = D | (N & present_state[0] & ~ present_state[1]);
assign next_state[0] = (N & present_state[1]) | (N & ~present_state[0])
    | (~N & present_state[1] & present_state[0]);

assign P = present_state[1];
assign C = present_state[1] & present_state[0];

endmodule
```

# Solution 2

```
module vending_machine2(input N, input
D, input clk, input reset_n, output P,
output C);
reg [1:0] next_state, present_state;
//Define states and state names
localparam [1:0] S0 = 2'b00, S5 =
2'b01 , S10 = 2'b10, S15 = 2'b11;

//Implement next states (combinational)
always @ (*)
begin
case (present_state)
S0: begin
if ({N,D}== 2'b00)
next_state = S0;
else if ({N,D}== 2'b01)
next_state = S10;
else
next_state = S5;
end
S5: begin
if ({N,D}== 2'b00)
next_state = S5;
else if ({N,D}== 2'b01)
next_state = S15;
else
next_state = S10;
end
end
```

```
S10: begin
if ({N,D}== 2'b00)
next_state = S0;
else if ({N,D}== 2'b01)
next_state = S10;
else
next_state = S5;
end
S15: begin
if ({N,D}== 2'b00)
next_state = S0;
else if ({N,D}== 2'b01)
next_state = S10;
else
next_state = S5;
end
endcase //end of case
end //end of always@(*)

// Implement flip-flops (sequential)
always @(posedge clk, negedge reset_n)
begin
if(reset_n==1'b0)
present_state <= S0;
else
present_state <= next_state;
end

//Note ordering of combinational and
sequential always blocks does not
matter
```

## Solution 2 – Cont'd

```
//specify the outputs
```

```
assign P = (present_state == S15) | (present_state == S10) ;
```

```
assign C = (present_state == S15);
```

```
endmodule
```

```
//specify the outputs (alternative method)
```

```
always @ (*)
```

```
begin
```

```
    case(present_state)
```

```
        S0: {P,C}= 2'b00;
```

```
        S5: {P,C}= 2'b00;
```

```
        S10: {P,C}= 2'b10;
```

```
        S15: {P,C}= 2'b11;
```

```
    endcase
```

```
end
```

```
endmodule
```

How did we handle the don't cares  
when input ({N,D}) is 2'b11 ?



# Stretch Your Thinking

- Handling don't cares when  $\{N,D\} = 2'b11$

```
S15: begin
    if ({N,D}== 2'b00)
        next_state = S0;
    else if ({N,D}== 2'b01)
        next_state = S10;
    else
        next_state = S5;
end
```



```
localparam [1:0] SX = 2'bxx; //
define don't care state
S15: begin
    if ({N,D}== 2'b00)
        next_state = S0;
    else if ({N,D}== 2'b01)
        next_state = S10;
    else if ({N,D}== 2'b10)
        next_state = S5;
    else
        next_state = SX; // assign
to don't care state
end
```



```
S15: begin
    if ({N,D}== 2'b00)
        next_state = S0;
    else if ({N,D}== 2'b01)
        next_state = S10;
    else if ({N,D}== 2'b10)
        next_state = S5;
    else
        next_state = S0; // assign
to initial state (reset state)
end
```

Is SX really an  
additional state?

# Additional Coding Styles

**//Example shown before**

```
S15: begin
    if ({N,D}== 2'b00)
        next_state = S0;
    else if ({N,D}== 2'b01)
        next_state = S10;
    else if ({N,D}== 2'b10)
        next_state = S5;
    else
        next_state = S0;
end
```



**// Using case statements**

```
S15: begin
    case ({N,D})
        2'b00 : next_state = S0;
        2'b01 : next_state = S10;
        2'b10 : next_state = S5;
        default: next_state = S0;
    endcase
end
```



**// Using Conditional operator**

```
S15: begin
    next_state = ({N,D}== 2'b00)? S0:
                  (({N,D}== 2'b01)? S10:
                  (({N,D}== 2'b10)? S5: S0));
end
```

# Summary

- Combinational always block Vs. Sequential always block
- FSM design example
  - Assigning and using state labels
  - Handling don't care states
  - Different coding styles



# Appendix


## Mealy Type FSM for the Vending Machine

# Mealy Type State Diagram

Inputs: {N, D}

Nickel = 5¢, Dime = 10¢

Outputs: {P, C}

 

# State Table (Mealy)

Present State ( $Q_1 Q_0$ )	Input {N,D}	Next State ( $D_1 D_0$ )	Output {P,C}
S0 (00)	00	S0 (00)	00
	01	S10 (10)	10
	10	S5 (01)	00
S5 (01)	00	S5 (01)	00
	01	S15 (11)	11
	10	S10 (10)	10
S10 (10)	00	S0 (00)	00
	01	S10 (10)	10
	10	S5 (01)	00
S15 (11)	00	S0 (00)	00
	01	S10 (10)	10
	10	S5 (01)	00

$Q_1 Q_0 \backslash ND$	00	01	11	10
00	0	1	X	0
01	0	1	X	1
11	0	1	X	0
10	0	1	X	0

$Q_1 Q_0 \backslash ND$	00	01	11	10
00	0	0	X	1
01	1	1	X	0
11	0	0	X	1
10	0	0	X	1

# Logic Expressions

$$D_1 = D + NQ_0\overline{Q_1}$$

Next States

$$D_0 = NQ_1 + N\overline{Q_0} + \overline{N}\overline{Q_1}Q_0$$

$$P = D + NQ_0\overline{Q_1} = D_1$$

$$C = D\overline{Q_1}Q_0$$

Outputs

# Verilog - Solution 1 (Mealy)

```
module vending_machine(input N, input D, input reset_n, input clk,
output P, output C);
wire [1:0] next_state;
reg [1:0] present_state;

always @ (posedge clk, negedge reset_n) // Implement flipflops in one
always block.
begin
    if(reset_n==1'b0)
        present_state <= 2'b00;
    else
        present_state <= next_state;
end

// Implement combinational logic (logic expressions)
assign next_state[1] = D | (N & present_state[0] & ~ present_state[1]);
assign next_state[0] = (N & present_state[1]) | (N & ~present_state[0])
    | (~N & present_state[1] & present_state[0]);

assign P = D | (N & present_state[0] & ~ present_state[1]);
assign C = D & ~present_state[1] & present_state[0];

endmodule
```



# Verilog Solution 2 (Mealy)

```
module vending_machine2(input N, input D, input clk, input reset_n,
output reg P, output reg C);
reg [1:0] next_state, present_state;
//Define states and state names
localparam [1:0] S0 = 2'b00, S5 = 2'b01 , S10 = 2'b10, S15 = 2'b11;

//Implement next states and outputs(combinational)
always @ (*)
begin
case (present_state)
S0: begin
    case ({N,D})
        2'b00 : begin next_state = S0; {P,C} = 2'b00; end
        2'b01 : begin next_state = S10; {P,C} = 2'b10; end
        2'b10 : begin next_state = S5; {P,C} = 2'b00; end
        default: begin next_state = S0; {P,C} = 2'b00; end
    endcase
end
S5: begin
    case ({N,D})
        2'b00 : begin next_state = S0; {P,C} = 2'b00; end
        2'b01 : begin next_state = S15; {P,C} = 2'b11; end
        2'b10 : begin next_state = S10; {P,C} = 2'b10; end
        default: begin next_state = S0; {P,C} = 2'b00; end
    endcase
end
end
```

# Solution 2 – Cont'd (Mealy)

```
S10: begin
    case ({N,D})
        2'b00 : begin next_state = S0; {P,C} = 2'b00; end
        2'b01 : begin next_state = S10; {P,C} = 2'b10; end
        2'b10 : begin next_state = S5; {P,C} = 2'b00; end
        default: begin next_state = S0; {P,C} = 2'b00; end
    endcase
end
S15: begin
    case ({N,D})
        2'b00 : begin next_state = S0; {P,C} = 2'b00; end
        2'b01 : begin next_state = S10; {P,C} = 2'b10; end
        2'b10 : begin next_state = S5; {P,C} = 2'b00; end
        default: begin next_state = S0; {P,C} = 2'b00; end
    endcase
end
endcase //end of case
end //end of always@(*)

// Implement flip-flops (sequential)
always @(posedge clk, negedge reset_n)
    begin
        if(reset_n==1'b0)
            present_state <= S0;
        else
            present_state <= next_state;
        end
    end

endmodule
```